How to Build your Infrared or Switch Activated **Jumbo 7 Segment Display**

Pat McMahon-V1-20/2/2016

Design Brief - Using a Jumbo 7 Segment Display, build your own Infrared or Switch Activated Jumbo 7 Segment Display, to run from Pat's 14M2 Picaxe PCB.

Note- As the Jumbo 7 Segment Display needs ~8Volts before it lights up, you need to use a battery snap & a 9V battery on Pat's 14M2 Picaxe PCB, not 6V.

Switch Activated Jumbo 7 Segment Display



Infrared Activated Jumbo 7 Segment Display



Below are some of the Production Steps, Tick off each box as you complete a task and Document it.



Bend 7 Seg Jumbo legs over & out to seperate.

Tin the ends of each Leg.



Pink Orange Blue Yellow

Black Purple White Brown

Black (Loop)



(When viewed from the back)

Strip, Twist, Tin and attach coloured wires as below. Populate Pat's 14M2 PCB and solder on back.





Populate (with Infrared parts if required).

DURAT

Attach a 9V Battery Snap to Pat's PCB (not 6V Battery Box).



Attach wires from 7 Seg to Pat's PCB, as below.

Note– C.3 only for switch activated. Black (pinC.3) Yellow (pinC.0) g Black(Negative)



Orange (pin0) a Pink (pin1) b Brown (pin2) c White (pin3) d Purple (pin4) e Blue (pin5) f

If Switch Activated, attach 10K Resistor to stop Debounce

Tin the other ends of the coloured wires & snip.



<u>to C (common)</u> <u>Black(—) C.3</u> <u>& Red (+) to</u> <u>NO (normally open),</u> <u>on the microswitch.</u>

If Switch Activated, also attach another 10K Resistor,



between the power negative(—)and the C.3, on the back of the PCB.

- Power up the 14M2, attach your PCB and download cable to your computer & Program with the Picaxe "Programming Editor" for either your-
 - 1— Infrared Remote Controlled Jumbo 7 Segment Display.
 - 2 Switch Activated Jumbo 7 Segment Display.

Test with Micro Switch, if Switch Activated.

3— Or any other input device ie Light Dependant Resistor



Program with Picaxe "Programming Editor".

Test with Universal Remote, if Infrared.



Well Done!

You have successfully built , Programmed and Tested your 14M2 Picaxe Microcontroller & Jumbo 7 segment Display.